

## Chapter 6

Use with Section 3

## REINFORCEMENT

## ● Electric Circuits

Use the terms and statements from this box to complete the table.

amount of electric energy used by a device	a circuit that has more than one path for the electric current to follow
a circuit that has only one path for the electric current to follow	George Simon Ohm
kilowatt	kW
Ohm's law	$P = I \times V$
parallel	parallel circuit
power = current $\times$ voltage	series
series circuit	$V = I \times R$
voltage = current $\times$ resistance	W
watt	

### IMPORTANT FACTS ABOUT ELECTRIC CIRCUITS

**1. There is a relationship among voltage, current, and resistance in an electric circuit.**

Name of law:	
Discovered by:	
Expression of law:	
Equation:	

**2. There are two types of electric circuits.**

Two types of circuits:	1. 2.
Definitions of these circuits	1.  2.

**3. The electrical power of a circuit can be measured.**

Definition of electrical power:	
Unit of electrical power:	1. Name: 2. Abbreviation: 3. Term for 1000 units: 4. Abbreviation for 1000 units:
Determining the electrical power of a circuit:	1. Expression: 2. Formula: